

Achieve High DC Precision and Wide Large-Signal Bandwidth with Hi-Z Buffer

Sponsored by Texas Instruments: For high-speed data-acquisition systems such as oscilloscopes and active probes, a single-chip solution can replace many discrete components, including FETs, protection diodes, and transistors.

To reliably capture high-frequency signals and fast transient pulses, wide-bandwidth data-acquisition systems such as oscilloscopes and active probes require high-performance analog-front-end (AFE) signal chains.

These AFE signal chains must ensure a high signal-to-noise ratio, offer low noise and distortion, and deliver high dc precision. They also must present a high input impedance (Hi-Z) over a wide frequency range to the device under test. Texas Instruments' BUF802, an open-loop unity-gain buffer with a JFET-input stage, can help you achieve these goals.

Composite Loop-Based Circuit


As an alternative to using the BUF802, [you can use a discrete-buffer composite-loop architecture that interleaves low- and high-frequency signal chains](#), a complex approach that nevertheless helps illustrate the challenges involved. Figure 1 shows the discrete-component implementation of a composite-loop-based circuit. The low- and high-frequency signal chains provide, respectively, dc precision and a wide large-signal bandwidth.


The high-frequency path travels through capacitor C_{HF} to a discrete buffer. C_{HF} presents a high impedance to low frequencies, which therefore travel to the discrete buffer by way of the low-frequency path that includes a precision op amp.

Note that each path has a unique transfer function. A key challenge is to interleave the two transfer functions to produce a net transfer function that ensures a flat response over the circuit's frequency range of interest. This is especially the case at the mid frequencies, where both the high- and low-frequency paths contribute to the composite output.

Optimizing the two paths

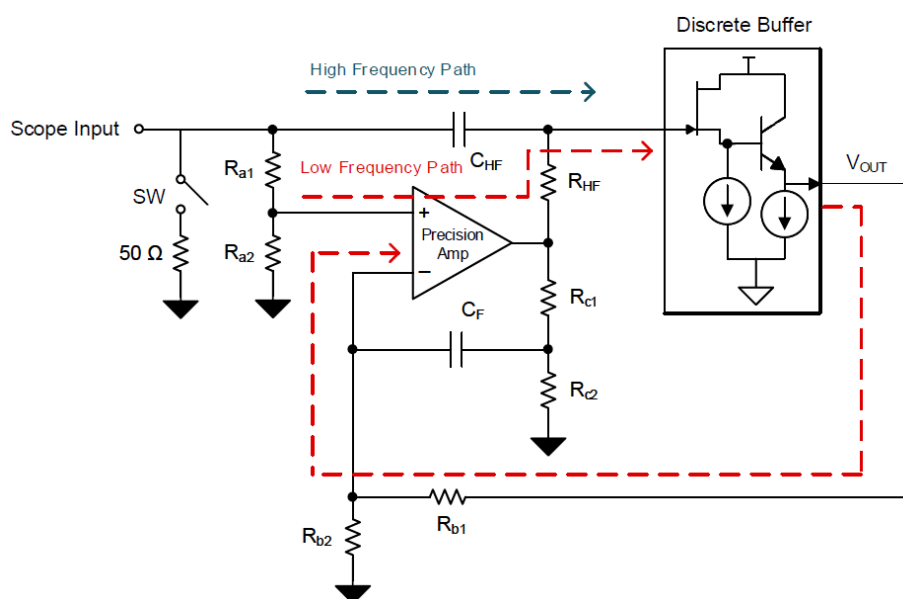1. The discrete-buffer composite-loop architecture interleaves low- and high-frequency signal paths.



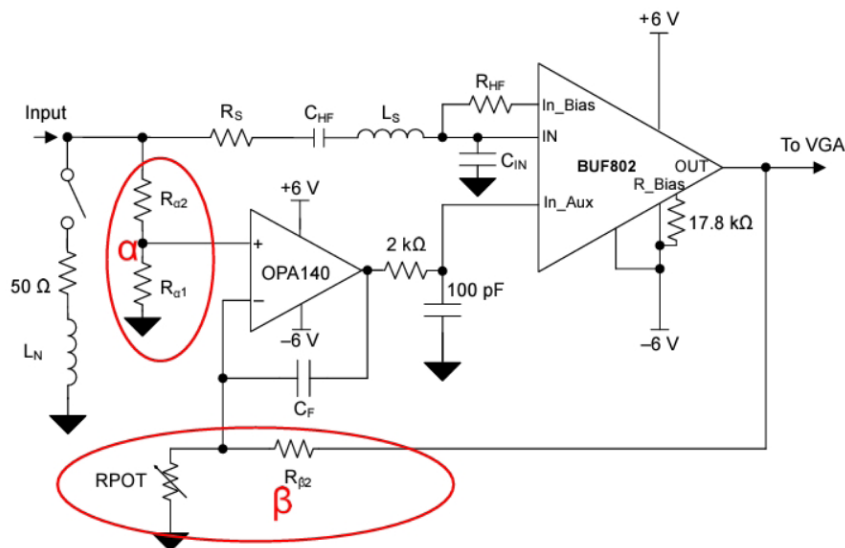

put (OUT) pin. Protection features such as input/output clamps help protect subsequent stages in the signal chain, thereby increasing system reliability.

Tuning AFE S-Parameters

[Use of the BUF802 simplifies the tuning of your AFE signal chain's S-parameters.](#) In turn, the composite circuit will be able to achieve a wide bandwidth and provide a smooth transition between low and high frequencies while reducing peaking in your circuit's frequency response.

First, consider S_{21} , the circuit's forward gain. Series input capacitor C_{HF} forms a voltage divider with the BUF802's input capacitance C_{IN} . To minimize the attenuation provided by this divider, make C_{HF} much

2. The BUF802 includes an auxiliary-path input (In_Aux).

can be challenging, too. You need to tune the passive-component values to obtain a flat response, maintain circuit stability, and keep the crossover frequency as high as possible to limit $1/f$ noise and provide for fast overdrive recovery. The interdependencies of the low- and high-frequency paths—with the same passive components C_{HF} and R_{HF} determining the poles of each path—can make these three goals difficult to achieve simultaneously.

JFET-Input Buffer

The BUF802 can assist you in reaching these goals. It offers a -3 -dB signal bandwidth of 3.1 GHz for 1-V p-p signals, a slew rate of 7,000 V/ μ s, an input impedance of 50 G Ω in parallel with 2.4 pF, and distortion of less than -41 dBc at 2 GHz. The BUF802 also can drive loads down to 50 Ω without the need for additional circuitry. The BUF802's 3- $\times$ 3-mm package easily fits within an active oscilloscope probe. [An evaluation board and oscilloscope reference design can help you adapt the BUF802 in your specific application.](#)


The BUF802 simplifies the process of obtaining a flat frequency response by minimizing the interdependencies of the low- and high-frequency paths. As shown in Figure 2, the BUF802 incorporates an auxiliary-path input (In_Aux) to which you connect the precision op amp's output. This connection establishes a composite loop while maintaining isolation between the low- and high-frequency paths.

The buffer also eliminates the need for several passive components—thereby simplifying the design—and permits a higher crossover frequency to minimize noise. The low- and high-frequency signal components recombine inside the BUF802, which presents the combined signal at its out-


greater than C_{IN} .

In addition, Figure 2 shows parasitic inductance L_S , which can interact with C_{IN} to form a resonant LC circuit that results in a peak in S_{21} at the resonant frequency. To reduce this peaking, minimize the trace lengths from circuit's input port to the BUF802's input. You can further reduce the peaking by increasing R_S , albeit at the cost of lower bandwidth (Fig. 3). The tradeoffs can be summarized as follows: increasing R_S protects the BUF802 and reduces peaking of S_{21} , while decreasing R_S increases bandwidth and reduces output noise.

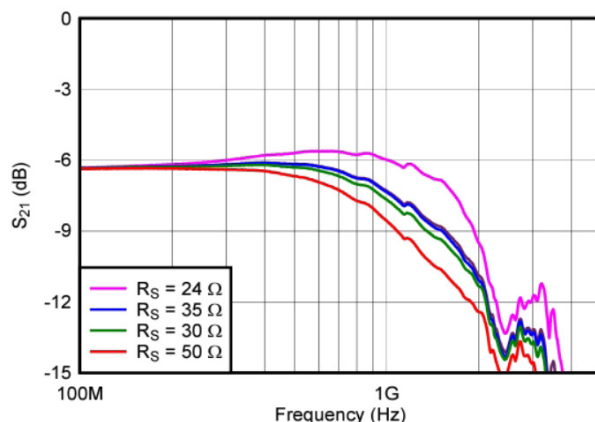To maintain a smooth transition from low frequencies to high frequencies, match the gain of the low-frequency and high-frequency paths. The gain of the low-frequency path is α/β , where:



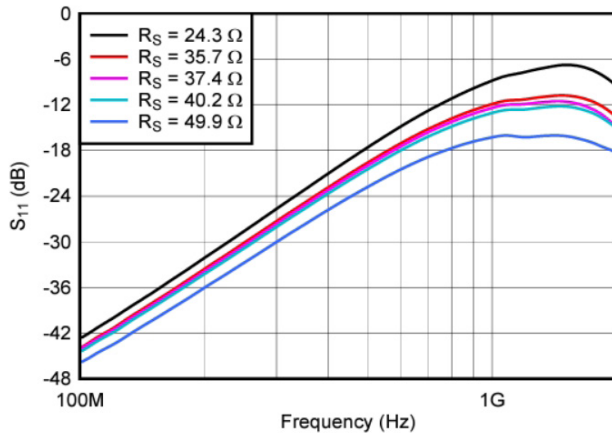3. Increasing R_S can reduce peaking in S_{21} , but it also lowers the bandwidth.



4. The value of R_S affects S_{11} .

$$\alpha = R_{\alpha 2} / (R_{\alpha 2} + R_{\alpha 1}) \text{ and } 1/\beta = 1 + (R_{\beta 2} / \text{RPOT})$$

The gain G of the high-frequency path is simply the gain of the BUF802, which can be read from the datasheet to be 0.96 V/V (typical). To maintain a constant S_{21} , adjust the value of RPOT to make $G = \alpha/\beta = 0.96$.

A smooth transition also requires that the high-frequency-response pole (f_{HF}) be much lower than the low-frequency pole (f_{LF}), defined as follows:

$$f_{\text{HF}} = 1 / (2 \times \pi \times R_{\text{HF}} \times C_{\text{HF}})$$

$$f_{\text{LF}} = \text{GBW} \times G_{\text{AUX}} \times \beta$$

where GBW is the gain bandwidth product of the precision amplifier.

Reflection Coefficient

Finally, consider S_{11} , the circuit's reflection coefficient. To minimize reflections and enhance signal integrity, target an S_{11} value of better than -15 dB across the frequency range of interest. A 50-Ω termination can help in achieving a suitable S_{11} , but you might want to provide for a high-impedance option for input signals that can't tolerate a 50-Ω load.

Because the JFET input of the BUF802 offers many gigaohms of impedance, a 1-MΩ termination won't affect overall performance. In addition, a 50-Ω termination can be switched in when needed, as shown in *Figure 2*.

Just as R_S affects S_{21} , it also affects S_{11} . Increasing R_S improves S_{11} at higher frequencies, while reducing R_S improves S_{11} at lower frequencies. *Figure 4* shows S_{11} for various values of R_S .

Conclusion

Designing an oscilloscope or data-acquisition-system AFE with a wide bandwidth and flat frequency response can be challenging. Texas Instruments' BUF802 open-loop unity-gain buffer plus associated evaluation board and reference design can help speed your way to success.